

## PLD Basics and Xilinx ISE tool flow

By

**K. Vasu**

Senior Application engineer  
[vasu@unistring.com](mailto:vasu@unistring.com), [vasu.vlsi@gmail.com](mailto:vasu.vlsi@gmail.com)

**Unistring Tech Solutions Pvt. Ltd**

# D10, 5th Floor, Eureka court, Beside Image hospitals, Ameerpet,  
 Hyderabad, ph:040-23732798, 09440318188  
[www.unistring.com](http://www.unistring.com)

**String Technologies**

#309, Vederi complex, opp Dilsukh Nagar bus Depot, Dilsukh nagar, Hyderabad,  
 ph: 040 - 24151900  
[www.stringtechnologies.net](http://www.stringtechnologies.net)

## What is programmable logic device (PLD) ?

- A device which comes with some generic (or) configurable hardware whose functionality can be changed as per the application
  - Different than microprocessors and DSPs
  - Useful when hardware solution is required but ASIC is not feasible
  - PALs, CPLDs and FPGAs are popular


## Programmable Logic Devices

- Sea of gates architecture (obsolete today)
- SPLDs (simple PLDs).
- CPLDs (complex PLDs).
- FPGAs (field programmable gate arrays).


## Sea of gates architecture




## SPLD basic Layout

 


- PAL, PLA and PROM

 

## PAL Architecture


 


## 22V10 PAL Logic Diagram

 

  
## Complex programmable logic device (CPLD)

Typically a CPLD consists of 50 SPLDs (An SPLD is a programmable logic array with AND and OR planes)



## Programmable Logic Array



Programmable interconnect matrix.

 

Each logic block is similar to a 22V10.

Figure 1. Ultra37128 Block Diagram

  Programmable devices containing repeated sections of small logic blocks



PLDs - Classification by Granularity

Granularity - What is the logic block size which is being configured

In general three different granularity classes can be found


- Small granularity (sea of gates architecture)
- Medium granularity (FPGA)
- Large granularity (SPLD and CPLD)

If the granularity is less then the effort required to synthesize and complete the wiring between the blocks is high.

If the granularity is high then while implementing a circuit the utilization of available programmable logic is less


## Xilinx tool flow for simulation and synthesis

## Xilinx Design Flow

 

 
## FPGA toolflow


- Hardware design is traditionally done by modeling the system in a hardware description language
- An FPGA “compiler” (synthesis tool) generates a netlist,
- which is then mapped to the FPGA technology,
- the inferred components are placed on the chip,
- and the connecting signals are routed through the interconnection network.



## HDL Synthesis

 

# Technology Mapping

 

17


# Download

- Once a design is implemented, you must create a file that the FPGA can understand
  - This file is called a bitstream: a BIT file (.bit extension)
- The BIT file can be downloaded directly into the FPGA, or the BIT file can be converted into a PROM file, which stores the programming information




19

# Place & Route

 

18

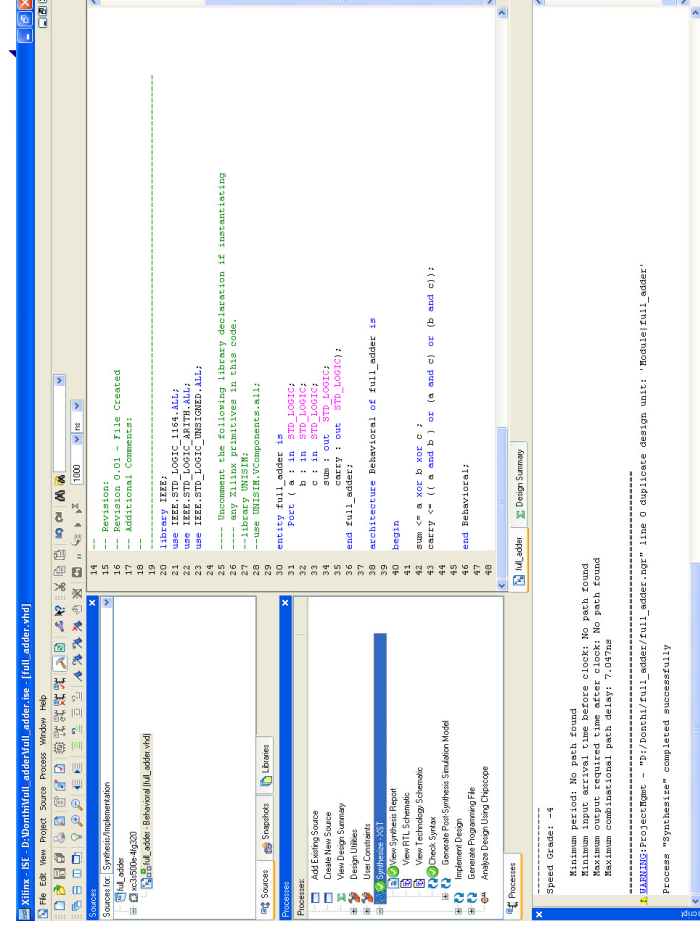

## ECAD lab syllabus & UTS FPGA board solutions

## ECAD lab syllabus

- Exp1: Various Digital Gates
- Exp2: DFF (7474)
- Exp3: Decade counter (7490)
- Exp4: 4 bit counter (7493)
- Exp5: shift register (7495)
- Exp6: Universal shift register (74194 / 74195)
- Exp7: 3 to 8 decoder (74138)
- Exp8: 4 bit comparator (7485)
- Exp9: 8 by 1 Multiplexer (74150)
- Exp10: 16 by 1 Multiplexer (74151)
- Exp11: RAM 16 by 1 - read and write operations (74189)
- Exp12: Stack and queue implementation using RAM

## UTS FPGA boards, softwares & IP cores

## Experiment – 1 Various digital gates

- VHDL coding, FPGA synthesis and on board verification of various digital gates.
- A simple 2 input AND gate will be explained here...
- Similarly the other gates can be tried out.

```
library ieee;
use ieee.std_logic_1164.all;

-----

entity AND_ent is
    port( x: in std_logic;
          y: in std_logic;
          F: out std_logic);
end AND_ent;


-----

architecture behav2 of AND_ent is
begin
    F <= x and y;
end behav2;


-----
```

```
-----

 architecture behav1 of AND_ent is
begin
    process(x, y)
    begin
        -- compare to truth table
        if ((x='1') and (y='1')) then
            F <= '1';
        else
            F <= '0';
        end if;
    end process;
end behav1;
```




 The output on kit can be observed with two pushbuttons and one LED as shown in the below figure.




- ## Experiment - 2
- VHDL coding, simulation and FPGA synthesis of Dual D type Flip Flop (7474).

LOGIC SYMBOL

 

IEC/IEEE SYMBOL

 

## VHDL code for exp-2

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity exp2_dual_diff is
Port ( SD0 : in STD_LOGIC;
      RD0 : in STD_LOGIC;
      CP0 : in STD_LOGIC;
      D0 : in STD_LOGIC;
      SD1 : in STD_LOGIC;
      RD1 : in STD_LOGIC;
      CP1 : in STD_LOGIC;
      D1 : in STD_LOGIC;
      Q0 : out STD_LOGIC;
      Q0_bar : out STD_LOGIC;
      Q1 : out STD_LOGIC;
      Q1_bar : out STD_LOGIC);
end exp2_dual_diff;
```


architecture Behavioral of exp2\_dual\_diff is

```
begin
FF1: process(SD0,RD0,CP0)
variable q_temp:std_logic;
begin
if SD0='1' then
q_temp := '1';
elsif RD0='1' then
q_temp := '0';
elsif CP0'event and CP0='1' then
q_temp := D0;
end if;
Q0 <== q_temp;
Q0_bar <= not q_temp;
end process;
```

```
FF2: process(SD1,RD1,CP1)
variable q_temp:std_logic;
begin
if SD1='1' then
q_temp := '1';
elsif RD1='1' then
q_temp := '0';
elsif CP1'event and CP1='1' then
q_temp := D0;
end if;
```


```
Q1 <== q_temp;
Q1_bar <= not q_temp;
end process;
```

end Behavioral;

 

 
## Experiment - 3

- VHDL coding, simulation and FPGA synthesis of the 7490 decade and binary counter



Let us continue remaining experiments in LAB

 The simulation results for test bench one will be as shown in the below figure.



BCD counter when R0\_1=0, R0\_2=0, R1\_1=0, R1\_2=0

Thank you  
(please fill the feedback form)